
EECS 427
Lecture 12: Multipliers
WH 11.9.1-11.9.3

1

Lecture Overview

- Multipliers are vital in digital signal processing and general purpose processors & GPUs
- They are speed limiting – very slow operations

2

Binary Multiplication

		1	0	1	0	1	0	Multiplicand (M-bits)		
x					1	0	1	1	Multiplier (N-bits)	
<hr/>										
					1	0	1	0	} Partial products	
				1	0	1	0	1		0
			0	0	0	0	0	0		
+		1	0	1	0	1	0			
<hr/>										
		1	1	1	0	0	1	1	0	Result

3


Key points

- MxN multiplication fits in N+M bits
- 2s complement multiplication is more difficult:
Either convert to + numbers and keep track of original signs OR use Booth's algorithm
- Major steps are:
 - 1) Partial product generation
 - 2) Partial product accumulation
 - 3) Final addition (done using fast carry lookahead techniques)

4

Generating Partial Products


- All partial products: AND

 

- Booth's recoding – reduction of partial product count (more later)


5

The Array Multiplier

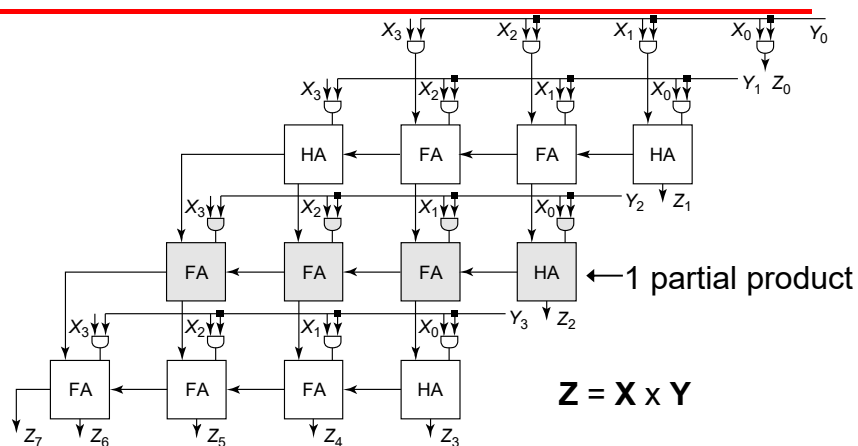

6

MxN Array Multiplier — Critical Path

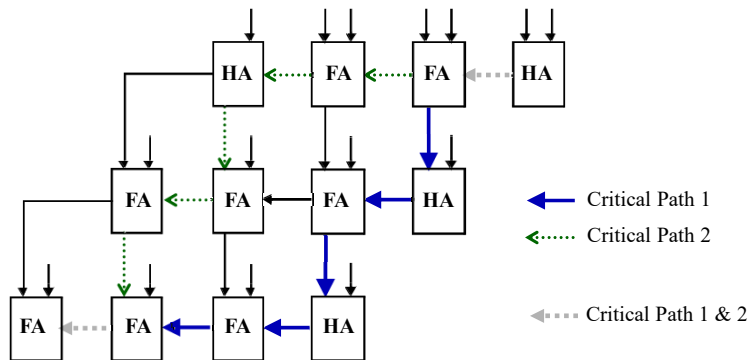


$$t_{mult} = [(M-1)+(N-2)]t_{carry} + (N-1)t_{sum} + t_{and}$$

Both carry and sum delays important: T-gate adder...

7

Carry-Save Multiplier

 

$$t_{mult} = (N-1)t_{carry} + t_{and} + t_{merge}$$

8

Booth Recoding

- To implement 2s complement multiplication, modified Booth recoding is typically used
- Idea: Recode the multiplier value in a higher radix in order to reduce the # of partial products
- Ex:

010111	(23)	
011110	(30)	
$\underbrace{}_1$ $\underbrace{}_3$ $\underbrace{}_2$		690

9

Modified Booth Recoding

- Now we need to be able to multiply by 0,1,2, or 3
 - +3 is not easy to implement; requires two stages (+4X – 1X OR +2X + 1X)
- Instead look at three bits at a time and use negatives:
 - $\pm 2X, \pm 1X, 0$
 - Must be able to multiply by 0, 1, 2, -1, -2
 - 0 and 1 are easy, 2X involves a shift left by 1 bit position, -1X: invert all bits and set Cin = 1, -2X: invert all bits, carry in a 1, and shift left by 1 bit

10

Recoding table

- From MSB to LSB, look at multiplier bits two at a time along with MSB of next less-significant pair
- Instead of 3Y, use $-Y$, then increment next partial product to add 4Y
- Similarly, for 2Y, use $-2Y$, then increment next partial product to add 4Y

$x_{i+2}x_{i+1}x_i$	Add to partial product
000	+0Y
001	+1Y
010	+1Y
011	+2Y
100	-2Y
101	-1Y
110	-1Y
111	-0Y

11

Example

- $$\begin{array}{r} 010111 \text{ (23)} \\ 011110 \text{ (30)} \\ \hline 690 \end{array}$$

Originally: 011110

011 $\rightarrow +2$

111 $\rightarrow 0$

100 $\rightarrow -2$

LSB extends with 0s

So we have:

$(+2)(0)(-2)$

12

Example, two 8-bit negative #'s

Extend sign in
partial products

$$\begin{array}{r}
 \text{X} \quad 10110010 = -78 \\
 \quad 10011101 = -99 \\
 \hline
 11111111110110010 \\
 000000010011110 \\
 111101100100 \\
 0010011100 \\
 \hline
 10001111000101010 = 7722
 \end{array}$$



Ignore carry out into 17th place

Recode:
10011101

13

Booth Decoding and Partial Product Generation


Operation	NEG	ZERO	TWO
x 0	0	1	0
x 1	0	0	0
x (-1)	1	0	0
x 2	0	0	1
x (-2)	1	0	1

  

14

Sign Extension

 
- Partial products can be negative
 - Require sign extension, which is cumbersome
 - High fanout on most significant bit



15

Simplified Sign Ext.

 
- Sign bits are either all 0's or all 1's
 - Note that all 0's is all 1's + 1 in proper column
 - Use this to reduce loading on MSB



16

Even Simpler Sign Ext.

 - No need to add all the 1's in hardware
 - Precompute the answer!



17

Summary

- Generally, multiply function consists of AND functions to generate the partial products and lots of addition
 - Carry and sum delays of adder cells can be equally critical
- Modified Booth recoding reduces the # of partial products to be added, improves speed
 - Also suitable for 2s complement addition
- Other topics:
 - Can pipeline within the multiplier unit to improve throughput
 - Tree structures to reduce the # of adders needed and speed the result (speed becomes logarithmic in # of bits); see Fig 11.85, Wallace Tree

18